
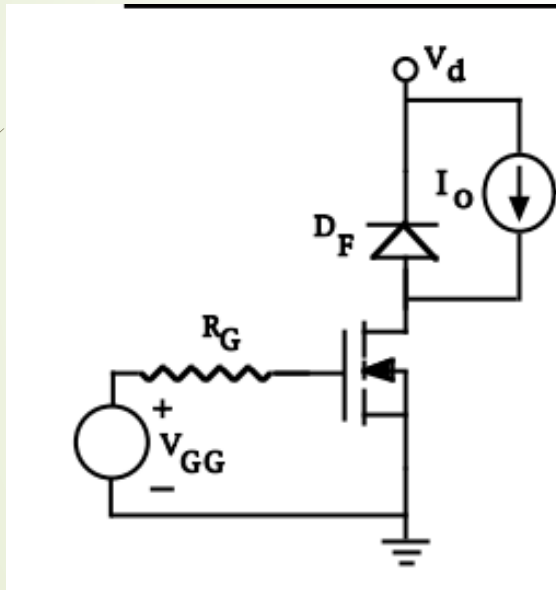



# POWER MOSFET SWITCHING CHARACTERISTIC

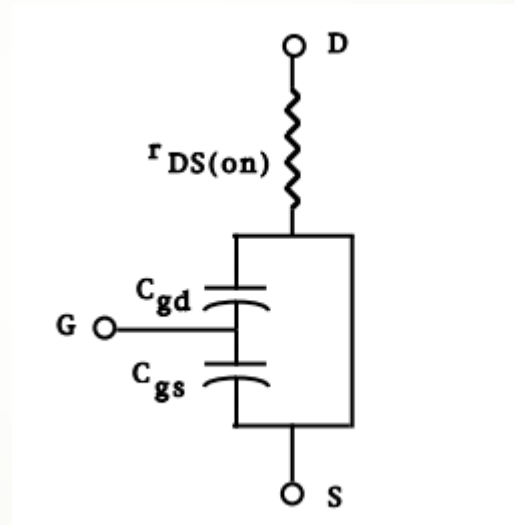

Buck Converter as Load



Triode Region Circuit Model

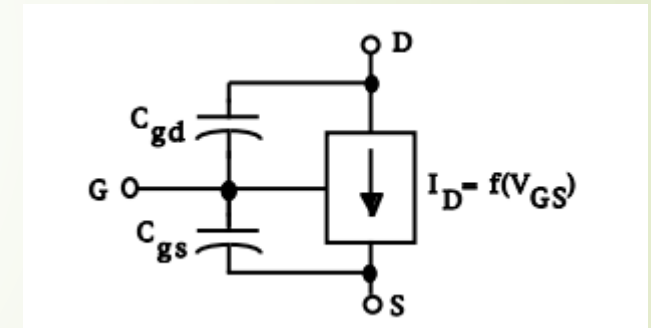


cut-off and Saturation Circuit Model

## ■ Switching Devices Categories:

Uncontrolled: Diodes

Semi controlled: Thyristors

Fully controlled/Controlled: Transistors



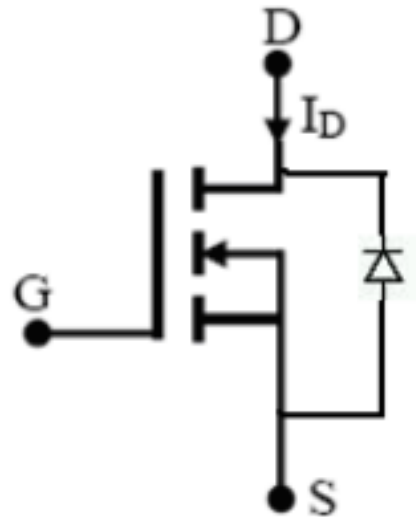


## ■ Ideal Switch

■ On-state :  $V_s=0$

■ Off-state:  $i_s=0$ ;

Thus, Power dissipation is zero.

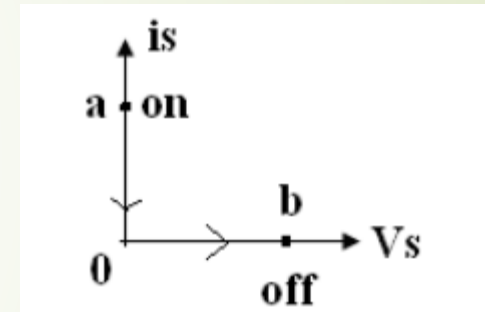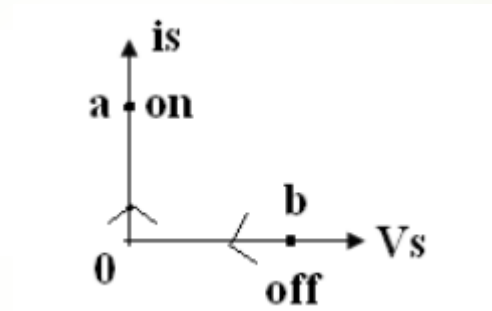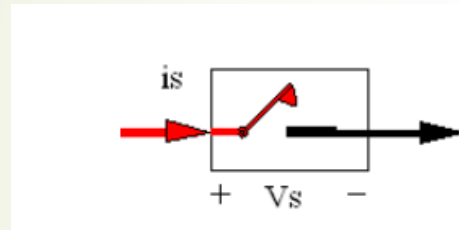





## ➤ Practical Switch


- Conduction Loss
- Blocking Loss
- Turn on Loss
- Turn of Loss
- Driver Circuit Loss
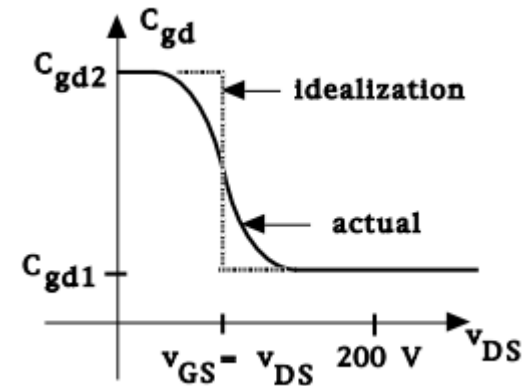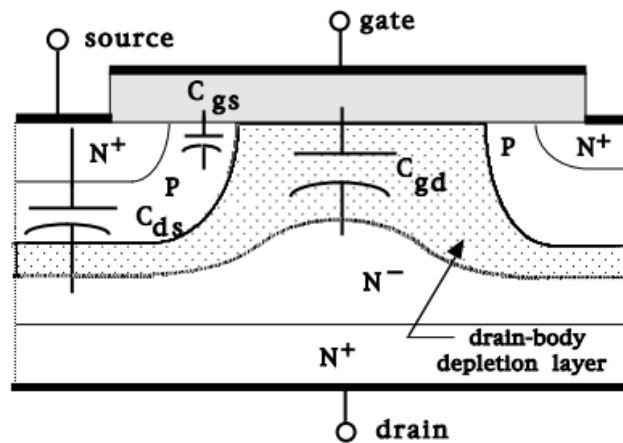
## ➤ Mosfet Capacitance


- $C_{gs}$  is almost constant
- $C_{gd}$  varies with  $V_{ds}$



### Input capacitance

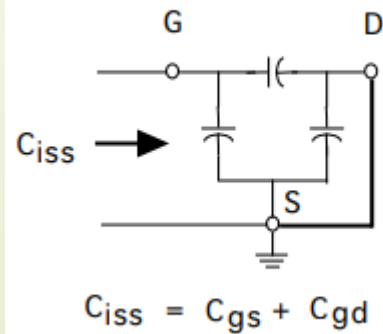


### Output capacitance

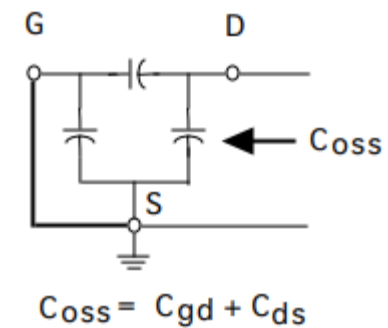

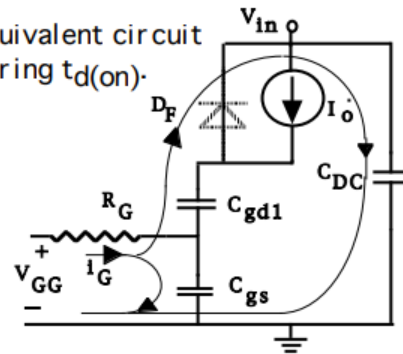
# Turn-on and Turn-off Equivalent Circuits


- Equivalent circuit during  $t_{d(on)}$ .




- Equivalent circuit during  $t_{ri}$ .

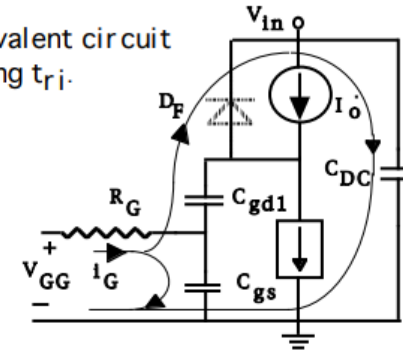


- Equivalent circuit during  $t_{fv1}$ .

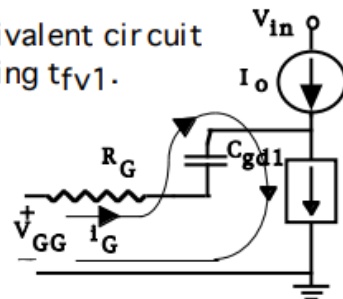


- Equivalent circuit during  $t_{fv2}$ .

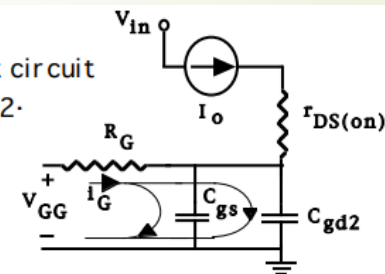


# Turn-on Waveforms

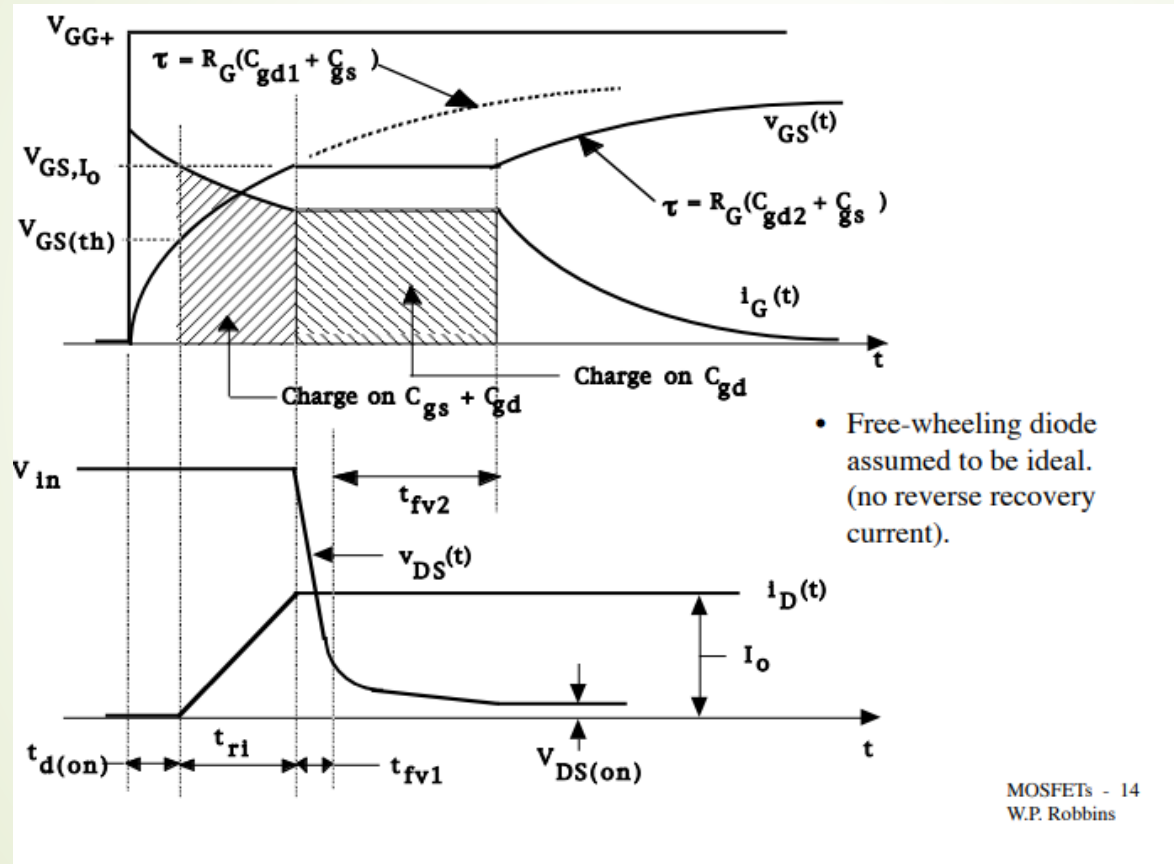

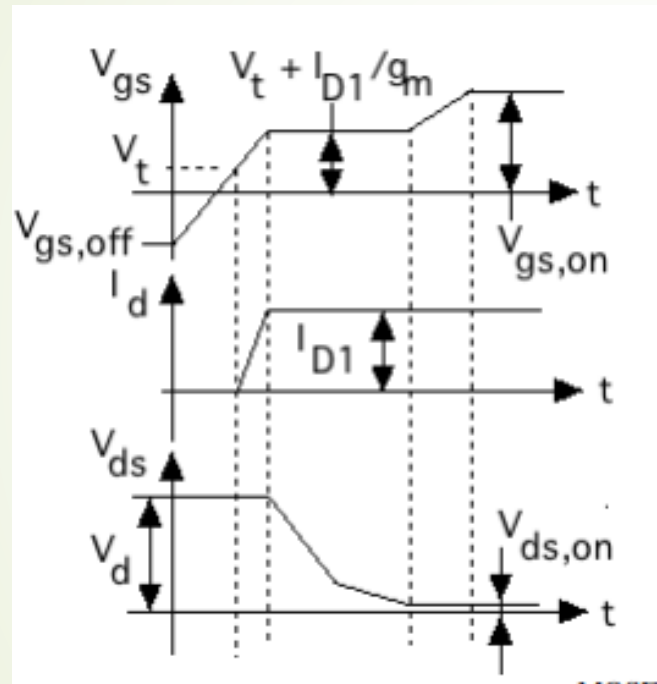



# Turn-off Waveforms

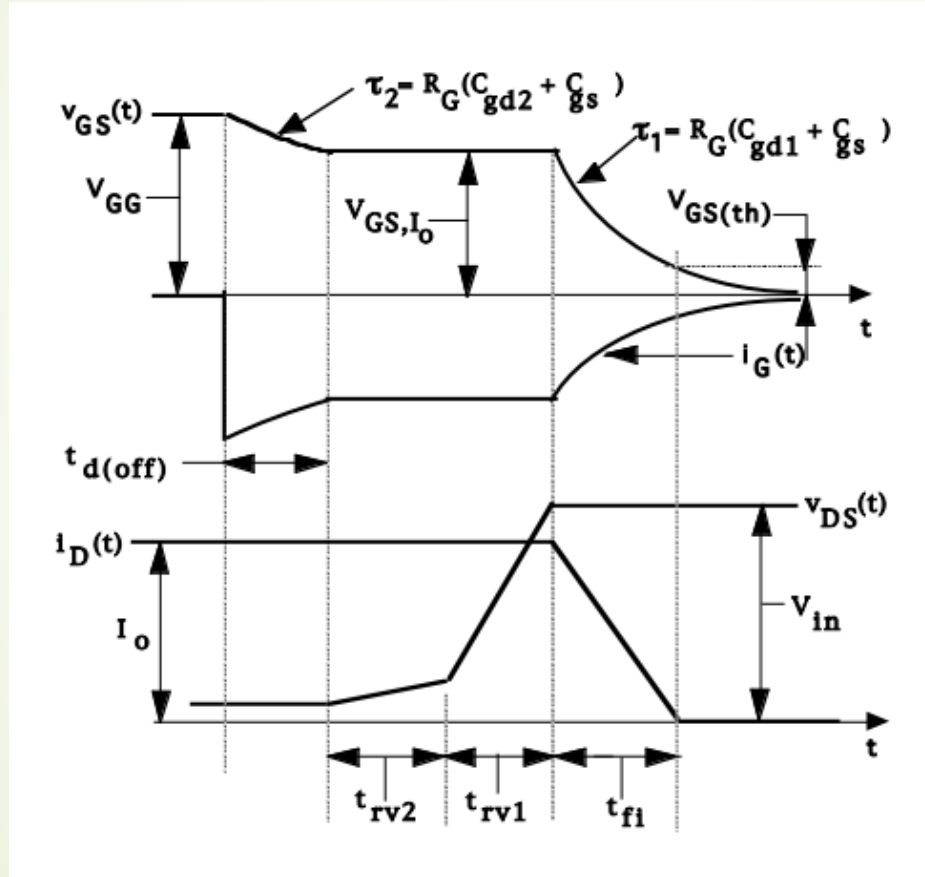



# On-state Losses

- $P_{on} = I_o^2 \cdot R_{ds(on)}$

- $R_{ds(on)}$  changes with  $V_{gs}$  and temperature

- 

Large  $V_{gs}$  make layer and channel resistances smaller.

If temperature increases,  $R_{ds(on)}$  increase. (Decreasing carrier mobility)