



Furkan Karakaya - 1937051

Muhammed Yusuf Candan - 1936541

# EE464 - Power Electronics 2

## Assignment #4

### 1) Step down converter:

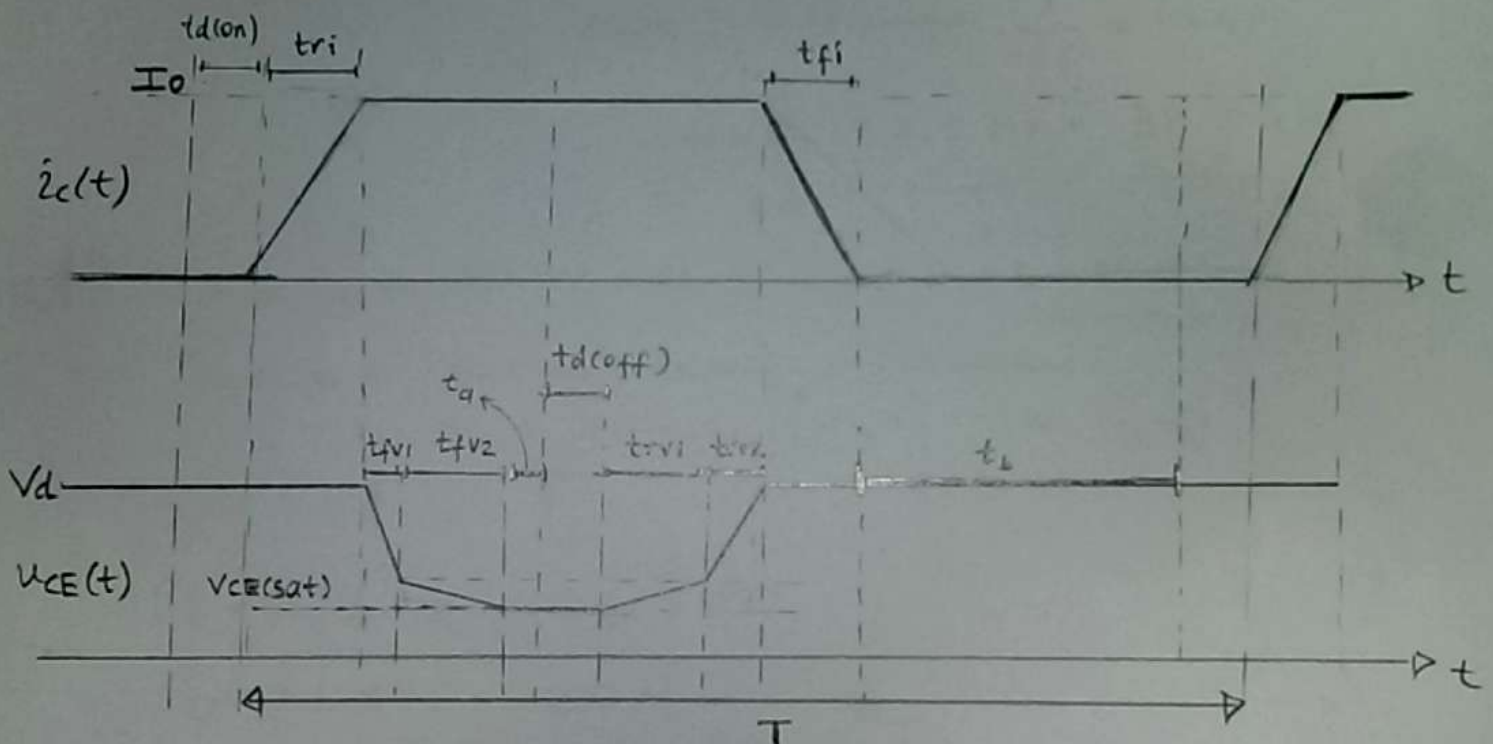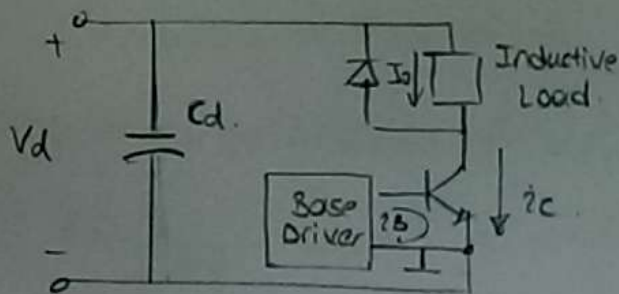

$$T = t_d(on) + t_{ri} + t_{fv1} + t_{fv2} + t_a + t_d(off) + t_{rv1} + t_{rv2} + t_{fi} + t_b$$

$$D = \frac{t_d(on) + t_{ri} + t_{fv1} + t_{fv2} + t_a}{T} = 0.5$$

$$t_d(on) + t_{ri} + t_{fv1} + t_{fv2} + t_a = t_d(off) + t_{rv1} + t_{rv2} + t_{fi} + t_b$$

$$t_a = t_b$$

$$\rightarrow T = 2 \times [100n + 200n + 50n + 50n + t_a]$$

$$T = 800n + 2t_a$$

$$E_{(on)} = \frac{I_o}{2} \cdot V_d \cdot t_{ri} + \frac{V_d + V_{CE(sat)}}{2} I_o (t_{fv1} + t_{fv2})$$

Note that, the voltage fall is assumed to be linear.

$$E_{(off)} = \frac{V_d + V_{CE(sat)}}{2} \cdot I_o \cdot (t_{rv1} + t_{rv2}) + \frac{I_o}{2} \cdot V_d \cdot t_{fi}$$

$$E_{(conduction)} = I_o \cdot V_{CE(sat)} \cdot (t_a + t_{d(off)}) = 80 \left( \frac{1}{2f} - 300n \right)$$

$$E_{(on)} = E_{(off)} = 604 \mu J$$

$$a.) P_{avg} = f (E_{(on)} + E_{(off)} + E_{(conduction)}) = f \times 1.208m + 40 + f \times 24\mu = 40 + f \times 1232\mu$$

$$\underline{P_{avg} = 40 + f \times 1232\mu}$$



$$b) P_{loss, max} = \frac{T_j - T_a}{R_{\theta ja}} = \frac{150 - 25}{1 \text{ } ^\circ\text{C/W}} = 125 \text{ W}$$

$$P_{avg} = 40 + f \times 1232 \mu = 125 \rightarrow f_{max} = 68994 \text{ Hz} \approx 69 \text{ kHz}$$

max permissible switch frequency  $\rightarrow$

$$c) E_{conduction} = E_{switching}$$

$$(t_a + t_{d(off)}) I_o \cdot V_{CE(sat)} = 2 \times \left[ \frac{V_d + V_{CE(sat)}}{2} \cdot I_o (t_{r1} + t_{r2}) + \frac{I_o}{2} V_d t_f \right]$$

$$80 \cdot \left( \frac{1}{2f} - 300 \text{ n} \right) = 2 \times 604 \text{ nJ}$$

$$\frac{1}{2f} - 300 \text{ n} = 15.1 \text{ n} \rightarrow \frac{1}{2f} = 15.4 \text{ n}$$

$$f = 32467.5 \text{ Hz} \approx 32.5 \text{ kHz}$$

$$d) P_{diode, avg} = I_o \cdot V_f \cdot (1-d) = 40 \cdot 1 \cdot 0.5 = 20 \text{ W}$$

$$P_{total, loss} = P_{diode, avg} + P_{switching} + P_{conduction}$$

$$= 20 + 40 + f \times 1232 \mu \quad \Big| \quad = 100 \text{ W}$$

$f = 32.5 \text{ kHz}$

$$P_o = I_o V_o, \quad V_o = D V_{in} = 50 \text{ V}$$

$$P_o = 40 \times 50 = 2000 \text{ W}$$

$$\eta = \frac{P_o}{P_o + P_{loss}} = 0.95$$

$$e) P_{total, loss} = 20 + 40 + f \times 1232 \mu \quad \Big| \quad = 145 \text{ W}$$

$69 \text{ kHz}$

$$\eta = \frac{P_o}{P_o + P_{loss}} = \frac{2000}{2145} = 0.93$$

e) Continue...

Diode power dissipation is constant while switch power dissipation is directly proportional with the switching frequency. Therefore, increased frequency causes a drop in the efficiency.

$$P_{out} = 2000 \text{ W}, \quad \eta = \frac{P_{out}}{P_{out} + P_{loss}}$$

$$P_{loss, \min} \Big|_{f=0} = 60 \text{ W} \quad \eta_{\max} = \frac{2000}{2000 + 60} = 0.971$$

Efficiency is less than 97.1%.

As indicated before, if the switching frequency is decreased, the efficiency increases. However, for lower frequencies, the current ripple becomes significant. So, for a acceptable current ripple (%), inductance, switching frequency and efficiency should be optimized.

$$\Delta I_L = \frac{1}{L} (V_d - V_o) d T_s = \frac{1}{L} \frac{V_d (1-d)}{f_s} d \Rightarrow L f_s = 62.5 \text{ for } \Delta I_L = 0.4 \text{ A} \text{ } \% \text{ ripple}$$


In market, 10 mH inductances can be found easily, so for this inductance value,  $f_s = 6.25 \text{ kHz}$ .

$$P_{loss} \Big|_{f_s = 6.25 \text{ kHz}} = 67.7 \text{ W} \Rightarrow \eta = 96.7\%$$

As a result, for such a converter whose efficiency is 97.1% maximum, 96.7% efficiency is acceptable and ripple is kept as also acceptable.



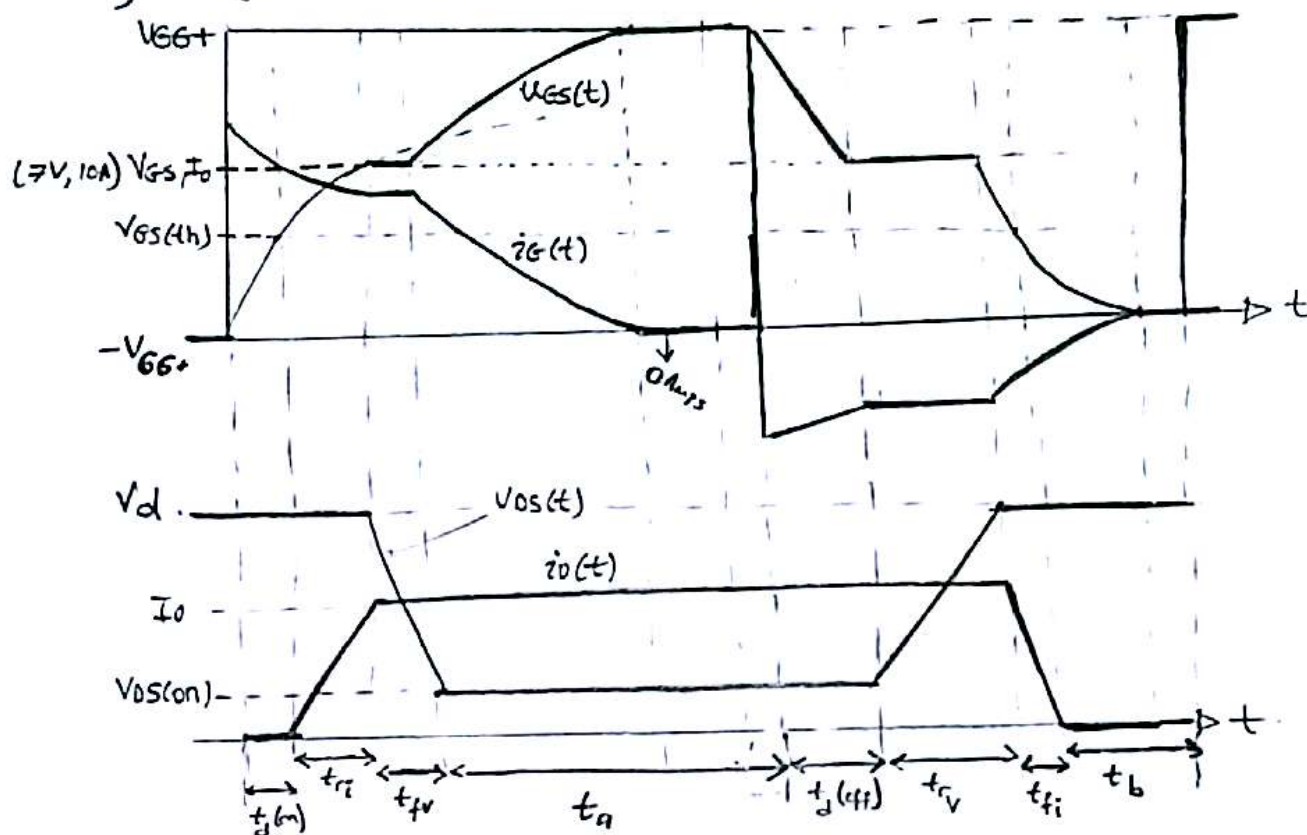- 2)  $V_d = 300V$ ,  $I_0 = 10A$ ,  $V_{GG} = \pm 15V$  % 50 duty cycle,  $R_g = 50\Omega$ ,  $V_{GS(th)} = 4V$ ,  $C_{gs} = 1nF$   
 a)  $C_{gd} = 150pF$ ,  $R_{ds(on)} = 0.5\Omega$



$$T = t_{d(on)} + t_{ri} + t_{fv} + t_a + t_{d(off)} + t_{rv} + t_{fi} + t_b$$


for  $t_{d(on)}$ ,  $V_{GS}(t) = V_{GS(th)} + (V_{GS(on)} - V_{GS(th)})e^{-t/\tau}$ ,  $\tau = R_g(C_{gs} + C_{gd}) = 57.5 ns$

$$V_{GS}(t) = V_{GS(th)} = 4V = 15 - 30e^{-t_{on}/57.5ns}$$

$$\Rightarrow t_{on} = 37.7 ns$$

for  $t_{ri}$ ,  $V_{GS} = 7V = 15 - 30e^{-(t_{on} + t_{ri})/57.5ns} \Rightarrow t_{ri} = 18.3 ns$

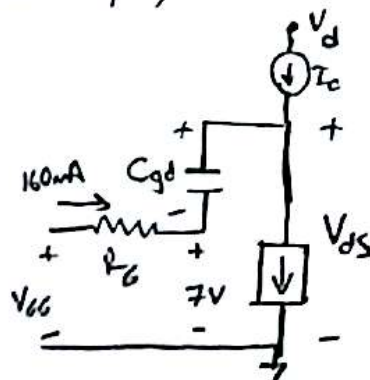for  $t_{fv}$ , it is assumed that the  $V_{DS}$  decreases linearly



$$V_{ds} = \underbrace{V_{GS(th)}}_{7V} + V_{Cgd}, \quad V_{ds(on)} = I_0 R_{ds(on)} = 5V$$

$$i_{Cgd} = C \frac{\partial V_{Cgd}}{\partial t} = C \frac{\partial (V_{ds} - 7V)}{\partial t} = C_{gd} \frac{300V - 5V}{t_{fv}}$$

$$t_{fv} = C_{gd} \frac{295V}{0.16A} = 276.6 ns$$

